
“MMC Multi-terminal HVDC” Lecture Report

Prof. Boon Teck Ooi, Dept. of Electrical Engineering McGill University, Montreal, Canada
2nd of July, 2014

Abel Ferreira

The modular multilevel converter topology offers great potential to a broad range of applications HVDC Transmission, FACTS, to motor drives due to lower switching losses compared to 2 level VSC topologies. Its mathematical model is continually being developed and, basically, operates as three independent single-phase ac/dc converters. Each of them is composed by a series connection of cells (also called submodules which are composed by an half bridge converter in parallel with a capacitor) with an inductor, as shown in figure 1a.

The operation of MMC is based on applying modulating signal $m_U(t)$ to the upper arm and $m_L(t)$ to the lower arm of each phase in the form of:

$$m_U(t) = \frac{1}{2} - \frac{U_{ref}}{U_{DC}} \cos(\omega t + \delta) \quad (1)$$

$$m_L(t) = \frac{1}{2} + \frac{U_{ref}}{U_{DC}} \cos(\omega t + \delta) \quad (2)$$

Applying these modulating signals to the correspondent arm's cells connects/bypasses a ratio of N capacitors as illustrated in figure 1b.

$$n_U(t) = N \left[\frac{1}{2} - \frac{U_{ref}}{U_{DC}} \cos(\omega t + \delta) \right] \quad (3)$$

$$n_L(t) = N \left[\frac{1}{2} + \frac{U_{ref}}{U_{DC}} \cos(\omega t + \delta) \right] \quad (4)$$

Summing (3) and (4) is clear that in each phase unit N cells are all the time connected.

The cell's status and their capacitor's voltages¹ over the time determines the converter upper- $u_U(t)$ and lower- $u_L(t)$ arm voltages.

$$u_U(t) = n_U(t)U_{cap}(t) \quad (5)$$

$$u_L(t) = n_L(t)U_{cap}(t) \quad (6)$$

The converter arm voltages are managed in order to achieve some goals as: the active/reactive power flow, the DC link voltage control, converter dynamics, etc.

¹ Considering that all the capacitors in the same arm balanced and equal to U_{cap}

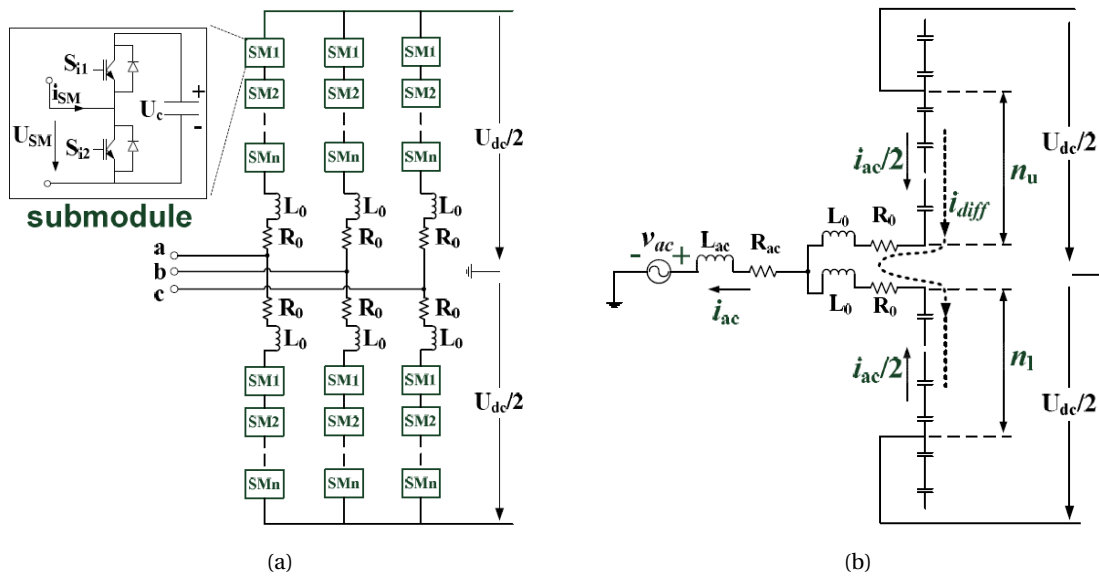


Figure 1: Three-phase MMC: (a) structure and (b) model